

# Homework Discussion, Week 4

Physics 1302

Dr. Andersen

## Chapter 21

32.) a) Since the resistors are in series, solve  $V = IR_{eq}$  for  $R_{eq}$ , then use  $R_{eq}$  to solve for  $R$ . b) Use  $V = IR$  for each. c) If  $V$  were larger, and  $I$  remained the same (the textbook author doesn't explicitly say that in the statement of the problem, but that is what he had in mind), then from  $V = IR$ , the resistance must be larger.

Answers: a)  $50 \Omega$ , b)  $1.8 \text{ V}$ ,  $8.5 \text{ V}$ ,  $7.8 \text{ V}$

37.) Start with the  $4.8$ ,  $3.3$ , and  $8.1$  in parallel. That equivalent resistance is in series with the  $6.3$ . That combination is in parallel with the  $1.5$  and  $2.5$ .

51.) (*Important notice about this problem: the answers in the back of the book are wrong! The correct answers are given below.*) a) I chose  $I_1$  to be the current through the  $9.8$  and  $3.9 \Omega$  resistors,  $I_2$  to be the current through the  $1.2 \Omega$  resistor, and  $I_3$  to be the current through the  $6.7 \Omega$  resistor. I also chose to draw  $I_1$  and  $I_3$  to be entering node A on the diagram, and  $I_2$  to be leaving the node. This gives a node equation at node A of:

$$I_1 + I_3 = I_2.$$

working clockwise around the left loop and the right loop gives loop equations:

$$12V - (3.9\Omega)I_1 - (1.2\Omega)I_2 - (9.8\Omega)I_1 = 0$$

and

$$(6.7\Omega)I_3 - 9.0V + (1.2\Omega)I_2 = 0.$$

These then need to be solved for the currents. b) Because point B is connected to the negative terminal of the 9 Volt battery, and point A is separated from point B by the  $1.2 \Omega$  resistor, point A must be at a higher potential. c) Note that the potential difference between A and B is just the potential difference across the  $1.2 \Omega$  resistor, so that the potential difference is just  $(1.2\Omega)I_2$ .

Answers a)  $I_1 = 0.72 \text{ A}$ ,  $I_2 = 1.75 \text{ A}$ ,  $I_3 = 1.03 \text{ A}$ . c)  $2.1 \text{ Volts}$ .

56.) a) Since the capacitors are in parallel, add the capacitances to get the equivalent capacitance. b) Because they are connected in parallel, the potential difference across each capacitor is equal. Since  $Q = CV$ , the capacitor

with the larger capacitance will be holding more charge. c) Plug and chug in  $Q = CV$ .

Answer: a)  $23 \mu F$  c)  $90 \mu C$  and  $180 \mu C$ .