

**ECE 3337 Summer-3 2016 Hebert, Homework 10 Due Tues 7/19**


**Problem 1.**

(a) Apply the initial value theorem and the final value theorem to  $F(s) = \frac{s+10}{s^2+3s+2}$

(b) Apply the initial value theorem and the final value theorem to  $F(s) = \frac{5}{(s+1)(s^2+9)}$

**Problem 2.** Given  $v_{in}(t) = e^{-3t}u(t)$ , find  $v_{out}(t)$  for the two circuits below by using circuit analysis in the LaPlace transform domain.

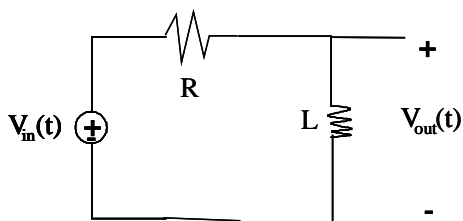(a)  $R = 10\ \Omega$ ,  $L = 3\ H$ , and the initial current through the 3 H inductor is  $i_L(0^-) = 1.0\ A$



(b) Again, the initial current through the 3 H inductor is  $i_L(0^-) = 1.0\ A$

