

**Problem 1.**

A balanced 3-phase system has a Y-connected source (voltage and impedance  $\tilde{V}_{a'n} = 1365\angle 0^\circ \text{ V}_{rms}$ ,  $Z_s = j2$ , positive phase sequence) connected to a transmission line (impedance  $Z_{line} = 1.5 \Omega$ ) which is connected to an **ideal** step-down three-phase  $Y - \Delta$  connected transformer ( $N_1 = 4000, N_2 = 2000$ ) whose secondary is connected to a Y-connected load ( $Z_{L-Y} = 85.5 + j114 \Omega$ ). Find the phase current in the secondary coil and total power delivered to the 3-phase load.

**Problem 2.**


A balanced 3-phase system has a three-phase Y-connected source (voltage and impedance  $\tilde{V}_{a'n} = 1365\angle 0^\circ \text{ V}_{rms}$ ,  $Z_s = j2$ , positive phase sequence) connected to a three-phase transmission line (impedance  $Z_{line} = 1.5 \Omega$ ) which is then connected to an **ideal** three-phase Y-Y step-down transformer ( $N_1 = 4000$ ). The voltage across the Y-connected load on the secondary side of the transformer ( $Z_{L-Y} = 85.5 + j114 \Omega$ ) is  $220 \text{ V}_{rms}$ . Find the number of turns  $N_2$  in the secondary windings.

**Problem 3.**

Consider a balanced 3-phase system with a Y-connected source having internal impedance  $Z_s = 4 \Omega$  connected to a 3-phase transmission line having impedance  $Z_{line} = 6 + j8 \Omega$ . The three-phase transmission line is connected to an **ideal** 3-phase transformer whose primary and secondary number of turns are  $N_1 = 4000$  and  $N_2 = 2000$ . The secondary side of the 3-phase transformer is connected to a Y-connected load  $Z_{Y-load} = 10 + j4 \Omega$ . Determine which arrangement of the transformer leads would result in the most power delivered to the load?

(a)  $Y - \Delta$  (b)  $\Delta - Y$  (c)  $\Delta - \Delta$  or  $Y - Y$

**Problem 4.**

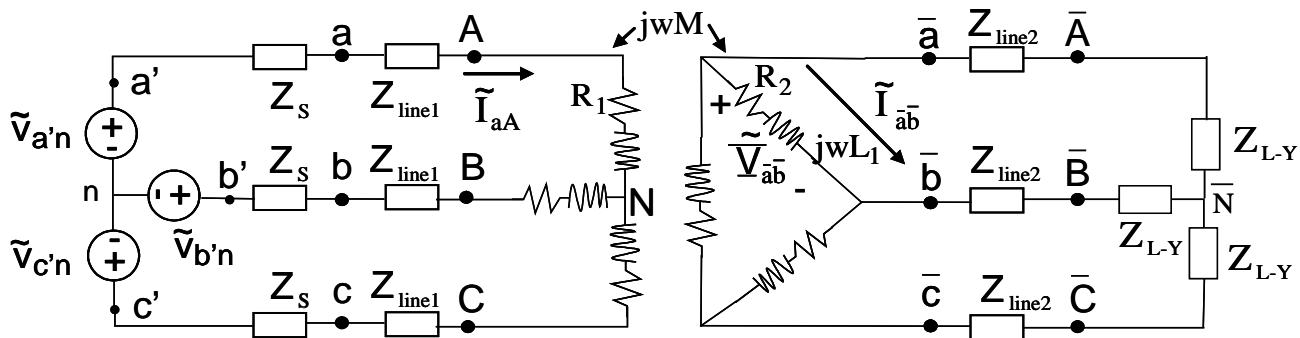

Given the balanced 3 phase circuit with a three phase  $Y - \Delta$  transformer above:

$$\tilde{V}_{a'n} = 1200\angle 0^\circ \text{ V}_{rms} \quad Z_s = 2 + j2 \quad R_1 + j\omega L_1 = 4 + j8 \quad R_2 + j\omega L_2 = 6 + j14$$

$$Z_{line1} = 10 + j5 \quad Z_{line2} = 4 + j1 \quad Z_{L-Y} = 112 - j16$$

$$\omega M = 9$$

Find  $I_{\bar{a}\bar{b}}$ , the current in the secondary windings.